

Assignment 3 Report

Group member: Deependra Shukla

Group member: Suraj Kumar Prajapati

1. Write Verilog code for a mod 16 synchronous counter along with the test bench.

```

`include "tff.v"
module mode_counter(clk, reset, mode, counter);
parameter size=16;
input clk,reset,mode;
output wire [size-1:0]counter;
wire [size-1:0]qb;
wire [size-1:0] t;
wire inv_mode;
wire [size-2:0]adv1, adv2, xr;
assign t[0] =1'd1;

tff tff_inst1(clk,reset,t[0],counter[0],qb[0]);

genvar i;
for (i=1; i<size; i=i+1) begin

if (i==1) begin
    assign adv1[i-1] = counter[i-1] & ~mode;
    assign adv2[i-1] = qb[i-1] & mode;
    assign xr[i-1] = adv1[i-1] ^ adv2[i-1];
end

else begin
    assign adv1[i-1] = counter[i-1] & adv1[i-2];
    assign adv2[i-1] = qb[i-1] & adv2[i-2];
    assign xr[i-1] = adv1[i-1] ^ adv2[i-1];
end
    tff tff_inst2(clk,reset,xr[i-1],counter[i],qb[i]);
end

endmodule

```

```
`include "mode_counter.v"

module tb_model_counter();
  reg clk, reset, mode;
  wire [15:0] counter;

  mode_counter #(.size(16)) c1(clk, reset, mode, counter);

  initial begin
    clk <= 1;
    forever begin
      #1 clk <= ~clk;
    end
  end

  initial begin
    $monitor("counter=%d", counter);


    reset = 1'b1;
    mode = 1'd0;
    #2 reset = 1'b0;
    #29 mode = 1'd1;
    #29 $finish;

  end

  initial begin
    $dumpfile("out.vcd");
    $dumpvars;
  end
endmodule
```

```
counter= 0
counter= 1
counter= 2
counter= 3
counter= 4
counter= 5
counter= 6
counter= 7
counter= 8
counter= 9
counter= 10
counter= 11
counter= 12
counter= 13
counter= 14
counter= 15
counter= 14
counter= 13
counter= 12
counter= 11
counter= 10
counter= 9
counter= 8
counter= 7
counter= 6
counter= 5
counter= 4
counter= 3
counter= 2
counter= 1
counter= 0
```

Terminal Output:

 

2. Write Verilog code for a 4-bit universal shift register along with the test bench. Instead of writing the entire code into a single file, you have to create modules for the flip-flops and call them into your main file.

```

1  module univ_shift_reg (
2      input wire clk, rst,
3      input wire [1:0] ctrl,
4      input wire [3:0] d,
5      output wire [3:0] q
6  );
7
8  reg [3:0] r_current, r_next;
9  always @(posedge clk or posedge rst) begin
10     if (rst)
11         r_current <= 4'b0000;
12     else
13         r_current <= r_next;
14 end
15 always @* begin
16     case (ctrl)
17         2'b00: r_next = r_current;
18         2'b01: r_next = {r_current[2:0], d[0]};
19         2'b10: r_next = {d[3], r_current[3:1]};
20         default: r_next = d;
21     endcase
22 end
23 assign q = r_current;
24 endmodule

```

```

vcd info: dumpfile out.vcd opened for output.
ctrl = 11, input = 1010, output = xxxx
ctrl = 11, input = 1010, output = 1010
ctrl = 01, input = 1010, output = 1010
ctrl = 01, input = 1010, output = 0100
ctrl = 10, input = 1010, output = 0100
ctrl = 10, input = 1010, output = 1010
ctrl = 00, input = 1010, output = 1010
ctrl = 11, input = 1010, output = 1010
ctrl = 01, input = 1010, output = 1010
ctrl = 01, input = 1010, output = 0100
ctrl = 01, input = 1010, output = 0100
ctrl = 01, input = 1010, output = 1000
ctrl = 01, input = 1010, output = 1000
ctrl = 01, input = 1010, output = 0000
ctrl = 11, input = 1010, output = 0000
ctrl = 11, input = 1010, output = 1010
ctrl = 10, input = 1010, output = 1010
ctrl = 10, input = 1010, output = 1101
ctrl = 10, input = 1010, output = 1101
ctrl = 10, input = 1010, output = 1110
ctrl = 10, input = 1010, output = 1110
ctrl = 10, input = 1010, output = 1111
ctrl = 10, input = 1010, output = 1111
[Done] exit with code=0 in 0.042 seconds

```

